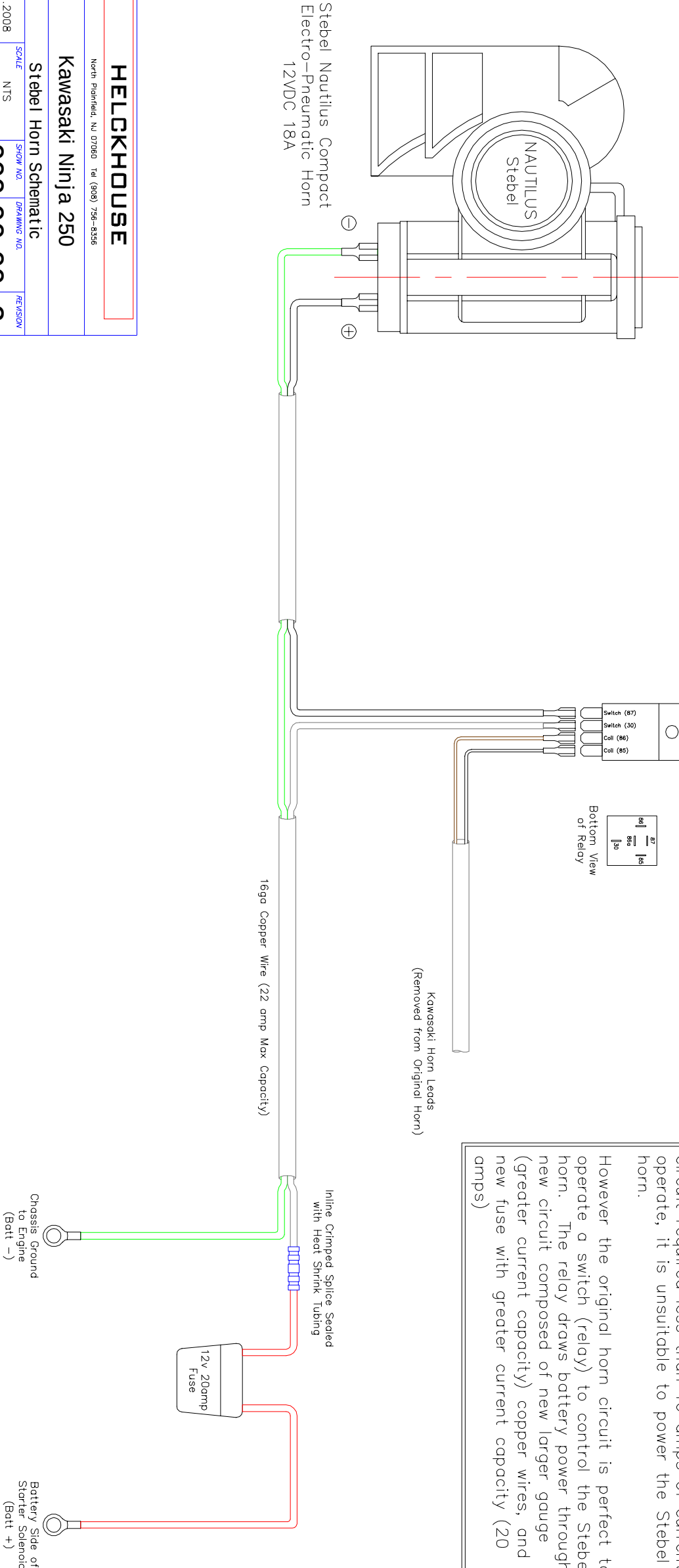


Stebel Nautilus Compact Schematic

Note: Seal all Crimped Terminals with Heat Shrink Tubing

HELCKHOUSE			
North Plainfield, NJ 07060 Tel (908) 756-8356			
Kawasaki Ninja 250			
Stebel Horn Schematic			
TITLE			
DATE	SCALE	SHEET NO.	DRAWING NO.
April, 2008	NTS		
DRAWN BY	DAVID	000 00.00	2



Why A Relay?

The Stebel horn requires 18 amps of battery power (current) to operate. As the original horn circuit required less than 10 amps of current to operate, it is unsuitable to power the Stebel horn.

However the original horn circuit is perfect to operate a switch (relay) to control the Stebel horn. The relay draws battery power through a new circuit composed of new larger gauge (greater current capacity) copper wires, and a new fuse with greater current capacity (20 amps)